

# RC circuit

Adapted from Wikipedia, the free encyclopedia

A **resistor–capacitor circuit (RC circuit)**, or **RC filter** or **RC network**, is an [electric circuit](#) composed of resistors and capacitors driven by a [voltage](#) or [current source](#). The *1st order RC circuit* composed of one resistor and one capacitor, is the simplest example of an RC circuit.

RC circuits, like other types of circuits, are used to "filter" a signal waveform, changing the relative amounts of low-frequency and high-frequency information in their output signals relative to their input signals. There are [high-pass filter](#) and [low-pass filter](#) and [band-pass filter](#) versions. A common application is for smoothing a signal, using a low-pass version.

## Introduction

There are three basic, linear passive [lumped analog circuit](#) components: the [resistor](#) (R), [capacitor](#) (C) and [inductor](#) (L). These may be combined in: the RC circuit, the [RL circuit](#), the [LC circuit](#) and the [RLC circuit](#) with the abbreviations indicating which components are used. These circuits, between them, exhibit a large number of important types of behaviour that are fundamental to much of [analog electronics](#). In particular, they are able to act as [passive filters](#). This article considers the RC circuit, in both [series](#) and [parallel](#) as shown in the diagrams.

## Natural response

The simplest RC circuit is a capacitor and a resistor in [series](#). When a circuit comprises only a charged capacitor and a resistor, then the capacitor would discharge its energy into the resistor. This voltage across the capacitor over time could be found through [Kirchhoff's current law](#), where the current coming out of the capacitor must equal the current going through the resistor. This results in the [linear differential equation](#)

$$C \frac{dV}{dt} + \frac{V}{R} = 0 .$$

If the capacitor voltage at time  $t = 0$  is  $V_0$ , solving this equation for the time-dependence of the voltage across the capacitor results in the exponential decay:

$$V(t) = V_0 e^{-\frac{t}{RC}} ,$$

where the time to fall to  $1/e$  of its initial value is called the *fall time*, *decay constant* or [time constant](#), given by

$$\tau = RC .$$

## Complex impedance

The [equivalent resistance](#) of a [capacitor](#) increases in relation to the amount of charge stored on the capacitor. If a capacitor is subjected to an [alternating current](#) voltage source, then the voltage of the capacitor would flip to the frequency of the AC voltage source. The faster the voltage of the AC voltage source flips, the less time charge would be allowed to be stored on the capacitor, therefore reducing the capacitor's equivalent resistance. This explains the [inverse](#) relationship the equivalent resistance of a capacitor has with the frequency of the voltage source.

The resistance, also known as the [complex impedance](#),  $Z_C$  (in [ohms](#)) of a capacitor with capacitance  $C$  (in [farads](#)) is

$$Z_C = \frac{1}{sC}$$

The [complex frequency](#)  $s$  is, in general, a [complex number](#),

$$s = \sigma + j\omega$$

where

- $j$  represents the [imaginary unit](#):

$$j^2 = -1$$

- $\sigma$  is the [exponential decay](#) constant (in [radians per second](#)), and
- $\omega$  is the [sinusoidal angular frequency](#) (also in radians per second).

## Sinusoidal steady state


Sinusoidal steady state is a special case in which the input voltage consists of a pure sinusoid (with no exponential decay). As a result,

$$\sigma = 0$$

and the evaluation of  $s$  becomes

$$s = j\omega$$

## Series circuit

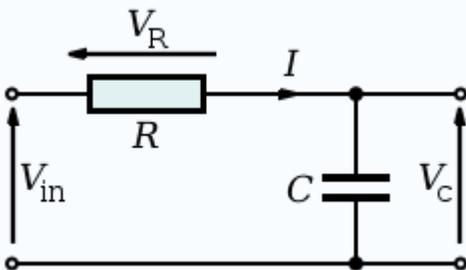

[Series](#) RC circuit

By viewing the circuit as a [voltage divider](#), the [voltage](#) across the capacitor is:

$$V_C(s) = \frac{1/Cs}{R + 1/Cs} V_{in}(s) = \frac{1}{1 + RCs} V_{in}(s)$$

and the voltage across the resistor is:

$$V_R(s) = \frac{R}{R + 1/Cs} V_{in}(s) = \frac{RCs}{1 + RCs} V_{in}(s)$$

## Transfer functions

The [transfer function](#) for the capacitor is

$$H_C(s) = \frac{V_C(s)}{V_{in}(s)} = \frac{1}{1 + RCs}$$

Similarly, the transfer function for the resistor is

$$H_R(s) = \frac{V_R(s)}{V_{in}(s)} = \frac{RCs}{1 + RCs}$$

## Poles and zeros

Both transfer functions have a single [pole](#) located at

$$s = -\frac{1}{RC}$$

In addition, the transfer function for the resistor has a [zero](#) located at the [origin](#).

## Gain and phase angle

The magnitude of the gains across the two components are:

$$G_C = |H_C(j\omega)| = \left| \frac{V_C(j\omega)}{V_{in}(j\omega)} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

and

$$G_R = |H_R(j\omega)| = \left| \frac{V_R(j\omega)}{V_{in}(j\omega)} \right| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}},$$

and the phase angles are:

$$\phi_C = \angle H_C(j\omega) = \tan^{-1}(-\omega RC)$$

and

$$\phi_R = \angle H_R(j\omega) = \tan^{-1}\left(\frac{1}{\omega RC}\right).$$

These expressions together may be substituted into the usual expression for the [phasor](#) representing the output:

$$\begin{aligned} V_C &= G_C V_{in} e^{j\phi_C} \\ V_R &= G_R V_{in} e^{j\phi_R}. \end{aligned}$$

## Current

The current in the circuit is the same everywhere since the circuit is in series:

$$I(s) = \frac{V_{in}(s)}{R + 1/Cs} = \frac{Cs}{1 + RCs} V_{in}(s)$$

## Frequency-domain considerations

These are [frequency domain](#) expressions. Analysis of them will show which frequencies the circuits (or filters) pass and reject. This analysis rests on a consideration of what happens to these gains as the frequency becomes very large and very small.

As  $\omega \rightarrow \infty$ :

$$\begin{aligned} G_C &\rightarrow 0 \\ G_R &\rightarrow 1. \end{aligned}$$

As  $\omega \rightarrow 0$ :

$$\begin{aligned} G_C &\rightarrow 1 \\ G_R &\rightarrow 0. \end{aligned}$$

This shows that, if the output is taken across the capacitor, high frequencies are attenuated (rejected) and low frequencies are passed. Thus, the circuit behaves as a [low-pass filter](#). If, though, the output is taken across the resistor, high frequencies are passed and low frequencies are rejected. In this configuration, the circuit behaves as a [high-pass filter](#).

The range of frequencies that the filter passes is called its [bandwidth](#). The point at which the filter attenuates the signal to half its unfiltered power is termed its [cutoff frequency](#). This requires that the gain of the circuit be reduced to

$$G_C = G_R = \frac{1}{\sqrt{2}}.$$

Solving the above equation yields

$$\omega_c = \frac{1}{RC} \text{ rad/s}$$

or

$$f_c = \frac{1}{2\pi RC} \text{ Hz}$$

which is the frequency that the filter will attenuate to half its original power.

Clearly, the phases also depend on frequency, although this effect is less interesting generally than the gain variations.

As  $\omega \rightarrow 0$ :

$$\begin{aligned} \phi_C &\rightarrow 0 \\ \phi_R &\rightarrow 90^\circ = \pi/2^c. \end{aligned}$$

As  $\omega \rightarrow \infty$ :

$$\begin{aligned} \phi_C &\rightarrow -90^\circ = -\pi/2^c \\ \phi_R &\rightarrow 0 \end{aligned}$$

So at [DC](#) (0 Hz), the capacitor voltage is in phase with the signal voltage while the resistor voltage leads it by 90°. As frequency increases, the capacitor voltage comes to have a 90° lag relative to the signal and the resistor voltage comes to be in-phase with the signal.

## Time-domain considerations


The most straightforward way to derive the time domain behaviour is to use the [Laplace transforms](#) of the expressions for  $V_C$  and  $V_R$  given above. This effectively transforms  $j\omega \rightarrow s$ . Assuming a [step input](#) (i.e.  $V_{in} = 0$  before  $t = 0$  and then  $V_{in} = V$  afterwards):

$$V_{in}(s) = V \frac{1}{s}$$


$$V_C(s) = V \frac{1}{1 + sRC} \frac{1}{s}$$

and
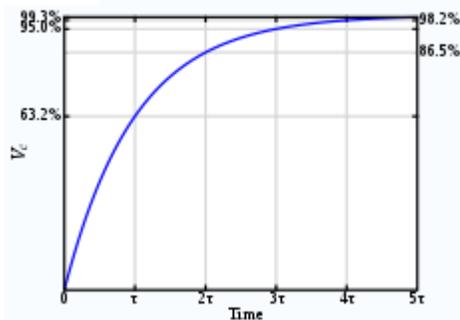
$$V_R(s) = V \frac{sRC}{1 + sRC} \frac{1}{s}$$



Capacitor voltage step-response.

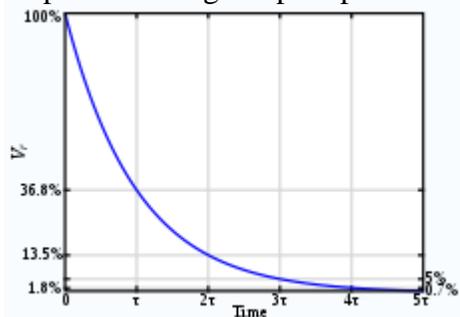

Resistor voltage step-response.

[Partial fractions](#) expansions and the inverse [Laplace transform](#) yield:

$$V_C(t) = V \left(1 - e^{-t/RC}\right)$$

$$V_R(t) = V e^{-t/RC}$$

These equations are for calculating the voltage across the capacitor and resistor respectively while the capacitor is [charging](#); for discharging, the equations are vice-versa. These equations can be rewritten in terms of charge and current using the relationships  $C=Q/V$  and  $V=IR$  (see [Ohm's law](#)).

Thus, the voltage across the capacitor tends towards  $V$  as time passes, while the voltage across the resistor tends towards 0, as shown in the figures. This is in keeping with the intuitive point that the capacitor will be charging from the supply voltage as time passes, and will eventually be fully charged and form an [open circuit](#).

These equations show that a series RC circuit has a [time constant](#), usually denoted  $\tau = RC$  being the time it takes the voltage across the component to either rise (across C) or fall (across R) to within  $1/e$  of its final value. That is,  $\tau$  is the time it takes  $V_C$  to reach  $V(1 - 1/e)$  and  $V_R$  to reach  $V(1/e)$ .

The rate of change is a *fractional*  $\left(1 - \frac{1}{e}\right)$  per  $\tau$ . Thus, in going from  $t = N\tau$  to  $t = (N + 1)\tau$ , the voltage will have moved about 63.2 % of the way from its level at  $t = N\tau$  toward its final value. So C will be charged to about 63.2 % after  $\tau$ , and essentially fully charged (99.3 %) after about  $5\tau$ . When the voltage source is replaced with a short-circuit, with C fully charged, the voltage across C drops exponentially with  $t$  from  $V$  towards 0. C will be discharged to about 36.8 % after  $\tau$ , and essentially fully discharged (0.7 %) after about  $5\tau$ . Note that the current,  $I$ , in the circuit behaves as the voltage across R does, via [Ohm's Law](#).

These results may also be derived by solving the [differential equations](#) describing the circuit:

$$\frac{V_{in} - V_C}{R} = C \frac{dV_C}{dt}$$

and

$$V_R = V_{in} - V_C.$$

The first equation is solved by using an [integrating factor](#) and the second follows easily; the solutions are exactly the same as those obtained via Laplace transforms.

### Integrator

Consider the output across the capacitor at *high* frequency i.e.

$$\omega \gg \frac{1}{RC}.$$

This means that the capacitor has insufficient time to charge up and so its voltage is very small. Thus the input voltage approximately equals the voltage across the resistor. To see this, consider the expression for  $I$  given above:

$$I = \frac{V_{in}}{R + 1/j\omega C}$$

but note that the frequency condition described means that

$$\omega C \gg \frac{1}{R}$$

so

$$I \approx \frac{V_{in}}{R} \text{ which is just } \text{Ohm's Law}.$$

Now,

$$V_C = \frac{1}{C} \int_0^t I dt$$

so

$$V_C \approx \frac{1}{RC} \int_0^t V_{in} dt,$$

which is an [integrator](#) across the capacitor.

### **Differentiator**

Consider the output across the resistor at *low* frequency i.e.,

$$\omega \ll \frac{1}{RC}.$$

This means that the capacitor has time to charge up until its voltage is almost equal to the source's voltage. Considering the expression for  $I$  again, when

$$R \ll \frac{1}{\omega C},$$

so

$$I \approx \frac{V_{in}}{1/j\omega C}$$
$$V_{in} \approx \frac{I}{j\omega C} \approx V_C$$


Now,

$$V_R = IR = C \frac{dV_C}{dt} R$$
$$V_R \approx RC \frac{dV_{in}}{dt}$$

which is a [differentiator](#) across the resistor.

More accurate [integration](#) and [differentiation](#) can be achieved by placing resistors and capacitors as appropriate on the input and [feedback](#) loop of [operational amplifiers](#).

## Parallel circuit

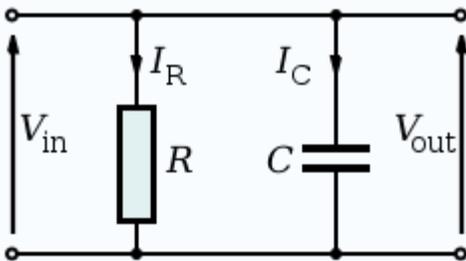

[Parallel](#) RC circuit

The parallel RC circuit is generally of less interest than the series circuit. This is largely because the output voltage  $V_{out}$  is equal to the input voltage  $V_{in}$  — as a result, this circuit does not act as a filter on the input signal unless fed by a [current source](#).

With complex impedances:

$$I_R = \frac{V_{in}}{R}$$

and

$$I_C = j\omega CV_{in}.$$

This shows that the capacitor current is  $90^\circ$  out of phase with the resistor (and source) current. Alternatively, the governing differential equations may be used:

$$I_R = \frac{V_{in}}{R}$$

and

$$I_C = C \frac{dV_{in}}{dt}$$